

Student name: _____

Karnaugh Maps

In an IB question you are typically given a scenario in which there are three possible inputs and you are told the outputs.
For example:

A register contains 3 binary values X, Y and Z (X is the MSB and Z the LSB):

X	Y	Z

When the binary number in this register is the equivalent of 1,3,5,6 or 7, the output is 1:

Complete the truth table for this system:

X	Y	Z	Outcome
0	0	0	0
0	0	1	1

What is the Boolean expression that this truth table represents?

Simplify the expression

Student name: _____

You may use a Karnaugh Map

	XY	00	01	11	10
Z					
0					
1					

Draw the corresponding circuit using only **and**, **or** and **not** gates.

A control system for a conveyor belt uses three sensors to detect the movement of the belt, the presence or absence of items on the belt and the press of a stop button by the operator. Each sensor X, Y and Z will send a 0 or a 1 to a 3-bit register with X as the MSB and Z as the LSB. Under the conditions corresponding to the equivalent decimal values of 1, 2, 5 and 6 a buzzer will sound.

Give the truth table for this system:

X	Y	Z	Buzzer

What is the expression?

Student name: _____

Simplify the Boolean expression for this truth table:

	XY	00	01	11	10
Z					
0					
1					


Construct the circuit:

Application of boolean logic to electronic circuit design.

Consider the addition of two binary numbers, A and B:

$$\begin{array}{r}
 \text{A} \quad 1 \quad 1 \quad 0 \quad 1 \\
 + \text{B} \quad 1 \quad 0 \quad 1 \quad 0 \\
 \hline
 \text{sum} \quad 0 \quad 1 \quad 1 \quad 0 \\
 \text{carry 1.}
 \end{array}$$

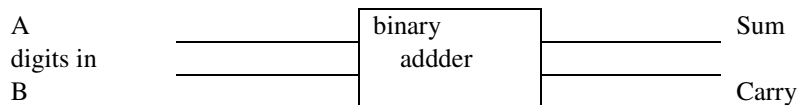A black box binary adder might work like this:



Expressed as a truth table it looks like this:


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Student name: _____

It is apparent that the Sum is A XOR B whereas the Carry is A AND B, expressed as boolean algebra:

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = A \cdot B$$

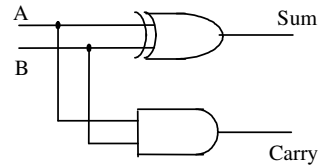


It is possible to construct a circuit from AND, OR and NOT gates

alone:

Full Adder

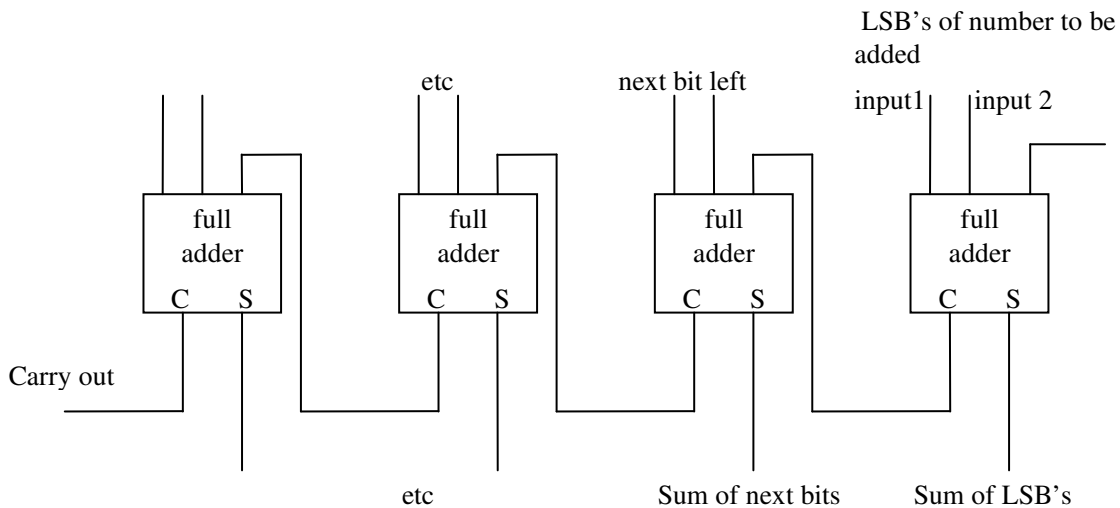
When adding binary numbers the carry must be added to the next column on the left, a full-adder is constructed from two half-adders:



A parallel adder for adding nibbles (4-bits or half a byte)


Student name: _____

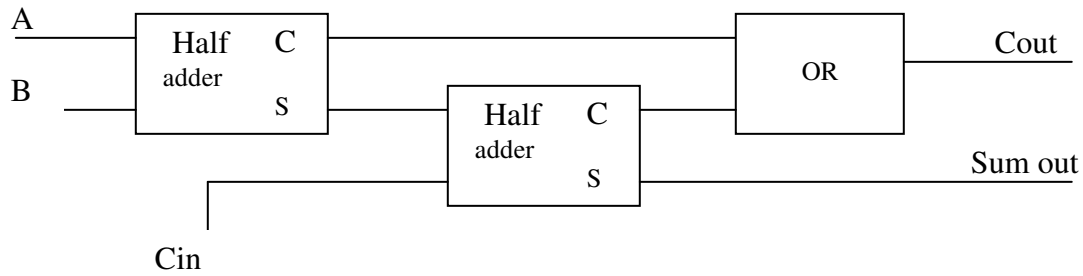A full adder is constructed from 2 half adders with the carry from each half adder going to an OR gate. Schematically:



What would a full-adder circuit look like? Draw it using XOR, OR and AND gates.

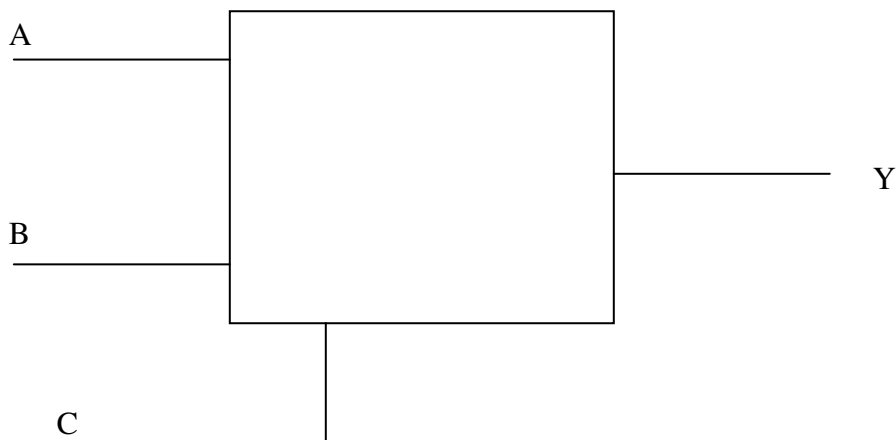The following schematic circuit is a 2-to-1 line multiplexer, if C is 0 then A Y=A else Y=B:



Student name: _____

Draw the truth table and construct the circuit using appropriate gates.

Design a circuit that compares three inputs A, B and C and whose output Y is a one if all inputs are equal.

Design a circuit that compares the same three inputs as above but outputs a one if any two out of the three inputs are the same.

Construct the truth table for both circuits.

Student name: _____

Laws of Boolean Algebra

1. Commutative laws

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

2. Associative laws

$$A + (B + C) = (A + B) + C \quad A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

3. Distributive laws

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C) \quad A + (B \cdot C) = (A + B) \cdot (A + C)$$

4. Tautology laws

(a) $A = A$

$$A + A = A$$

(b) $A + \text{NOT } A = 1$

$$A \cdot \text{NOT } A = 0$$

5. Absorption laws

$$A + (A \cdot B) = A$$

$$A \cdot (A + B) = A$$

6. Common sense laws

(a) $0 \cdot A = 0$

$$1 + A = 1$$

(b) $1 \cdot A = A$

$$0 + A = A$$

(c) $\text{NOT } 0 = 1$

$$\text{NOT } 1 = 0$$

7. Double complement law

$$\text{NOT NOT } A = A$$

8. De Morgan's law

$$(\text{NOT } A + \text{NOT } B) = \text{NOT } (A \cdot B)$$

$$(\text{NOT } A \cdot \text{NOT } B) = \text{NOT } (A + B)$$

(NOT the individual terms. Change the sign. NOT the lot)